
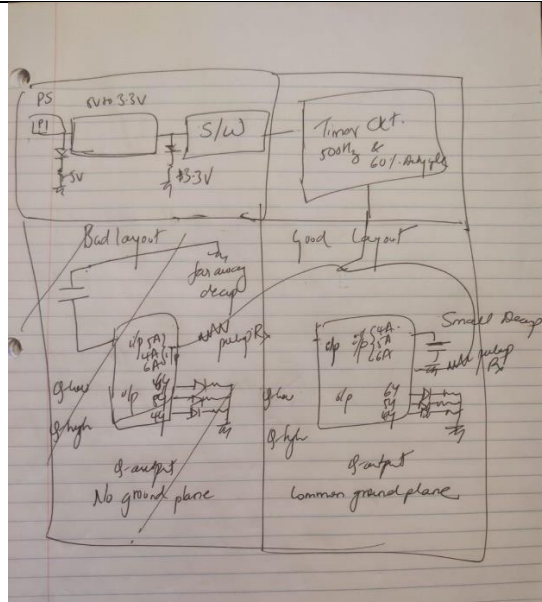
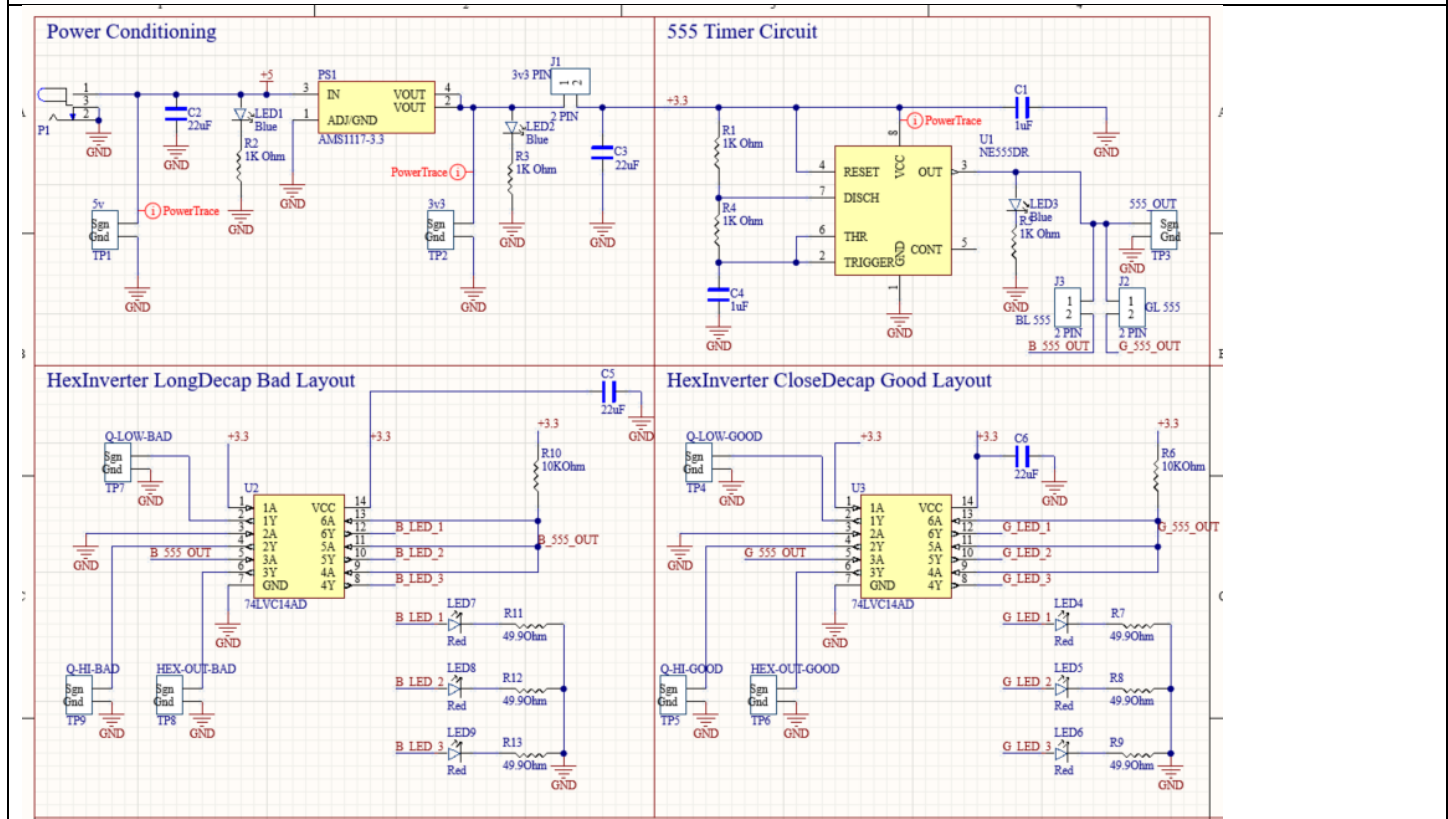


**Project Overview/Definition of work:**

There will be two designs integrated in one – Good Layout and Bad Layout for Hex-inverter driven by a 555 timer. The good layout would have a decoupling capacitor in proximity and a contiguous ground plane whereas a Bad layout would have decoupling capacitor placed far away as well only one via to the ground plane (no common ground plane). Significant parts are AMS1117 (5v to 3.3V regulator), 555 timer IC – Asynchronous mode (input clock source) and Hex-inverter (7414) to act as buffered system for output and addition of pull-up resistors so that pins do not float. The output of hex-inverter should be a opposite logic level of the input fed with a frequency of about 500 Hz and duty cycle of 60%.



**Napkin Sketch:****Schematic**

Sketch of schematic:

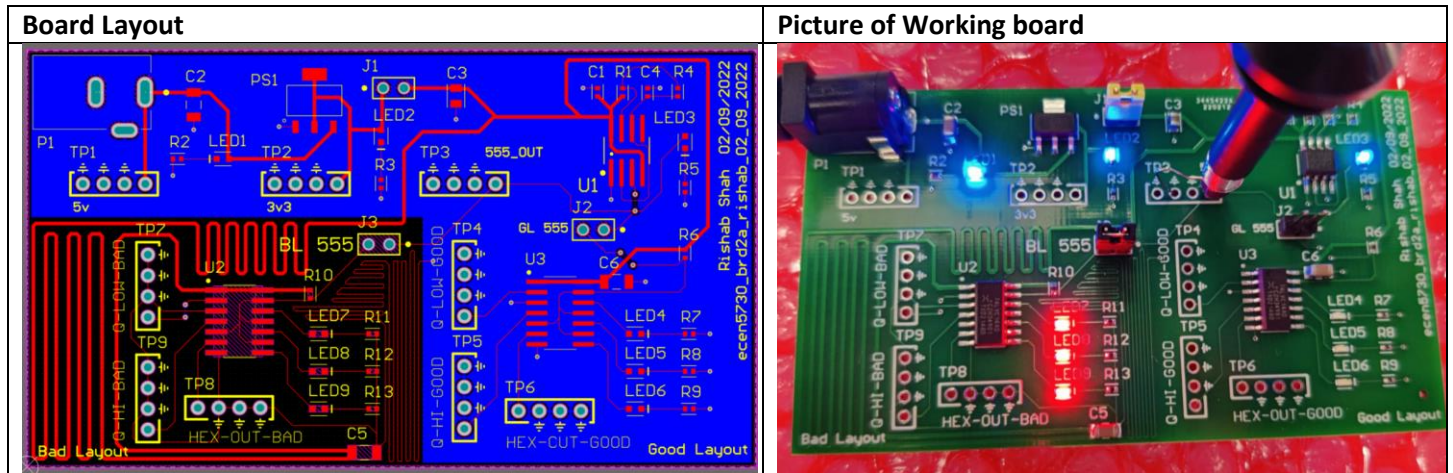

Measurements:

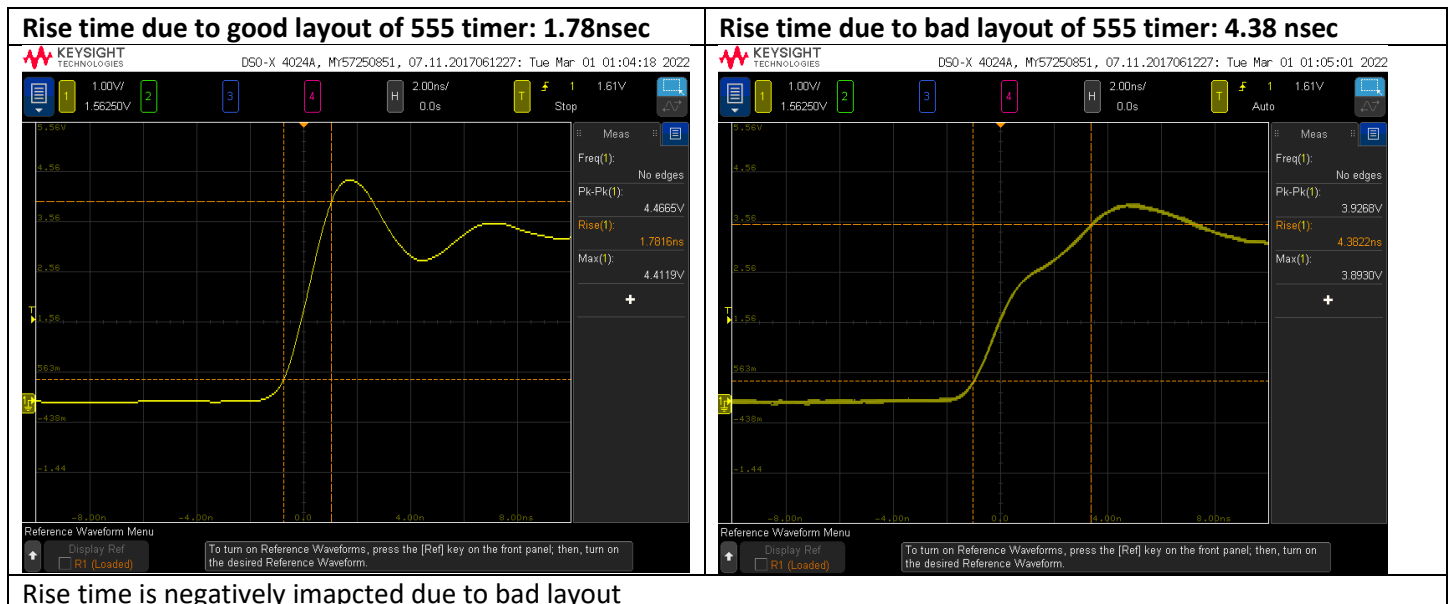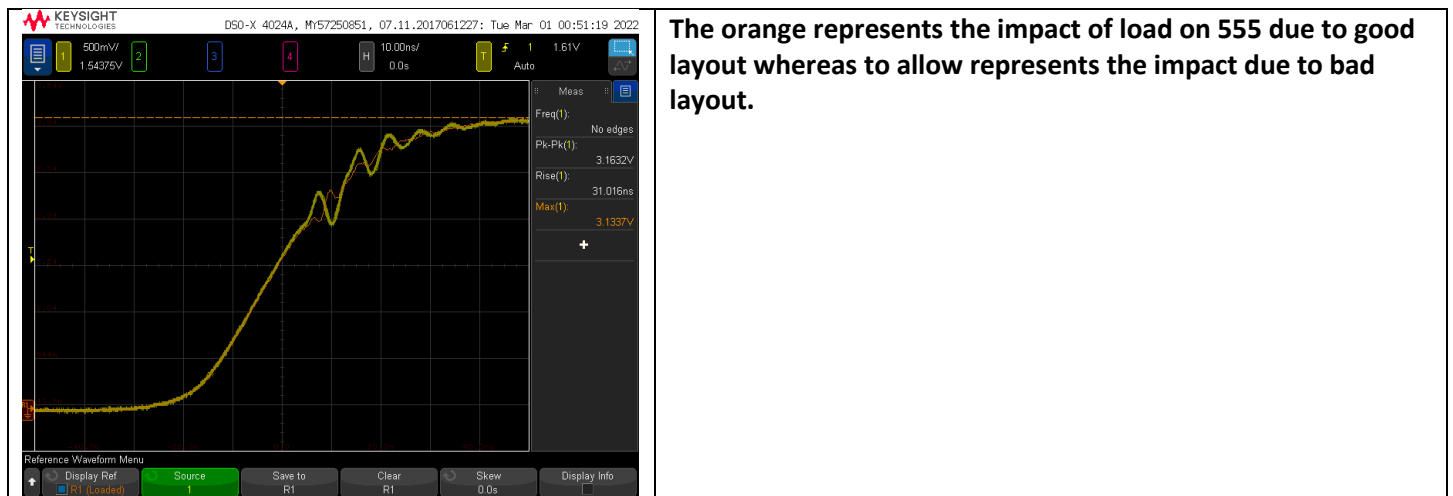a) Impact of load on 555 timer (input source) due to Bad and Good Layout:



Rise time is negatively impacted due to bad layout

*From the images, it is found that a poor layout of Hex inverter negatively affects the rise time of the signal which has a negative impact for high-speed electronics as the rise time is more.*

#### **Q-High and Q-Low significance for measurement of ground bounce:**


This is used for measurement between quiet output signal-return loop that is not switching and the other signal-return loops that switch and is used to measure ground noise/crosstalk.

These two pins are called quiet HIGH and quiet LOW because nominally, these pins are not switching, and they should have no changing voltage on them. Any voltage we measure must be switching noise.

#### **b) Q outputs on good and bad layouts:**


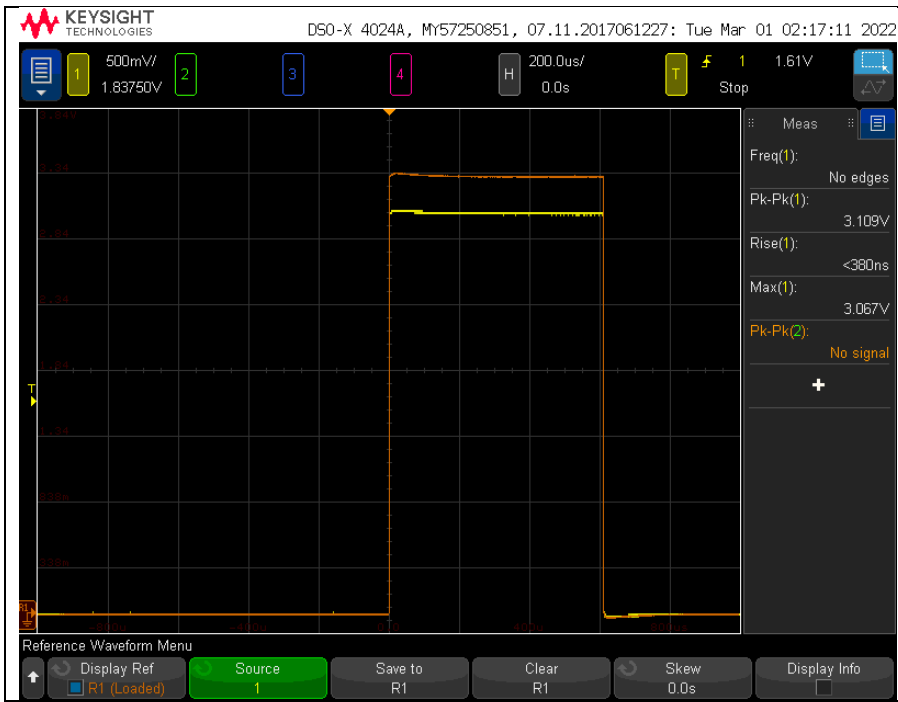
#### **C) Thevenin output resistance of the Hex inverter I/O: (Extra-Credit)**



Thevenin Output Resistance of the Hex-inverter (good Layout):

$V_{th} = 3.23V$

$V_I = 3.067$


$R_I = \text{LED} + \text{Resistor} = 50 \text{ Ohm (approx.)}$

$R_{th} = R_I * (V_{th} - V_I / V_I)$   
 $= 50 * (3.23 - 3.067 / 3.067)$   
 $= 2.657 \text{ Ohm}$

#### d) Switching noise on the 5 V and 3.3 V rails



 **The bad layout to some extent has a negative effect on the power rails. It is in mV but definite impact.**



**The bad layout to some extent has a negative effect on the power rails. It is in mV but definite impact.**

The noise on a 3.3 v rail is less compared to a 5v rail comparatively.

#### Demonstration of best design practices and best measurement practices:

Spring tips were used for measurement using CRO to reduce the inductance and decoupling capacitor was placed close to the power of the 555 IC.

The significance of selecting the signal to be **centered** for comparative analysis using Utility-> preferences


The average option from acquire is very useful as it eliminates stray noises and makes the signal cleaner to view.

#### Improvement/Care for next time:

To make use of common ground plane in future layouts as well as placement of the capacitor close to the controller.

Make use of 36mm as height and 6mm as width of stroke for all the silkscreen as they are readable and consume less space.

## Picture of Board:

 

## Analysis of your project:

Q. What worked and you did well and want to do in future design

- Labelling every component and division of the blocks beforehand helped to visualize and breakdown tasks.

Q. What did not work, and you will want to do differently in future designs.

- The noise contribution on good layout was more compared to the board which was analyzed in Lab 6.

Q. Were there any hard errors- why did they go wrong

- No hard errors

Q. Were there any soft errors that you would like to do differently next time?

- Continue using common ground plane and